

DIGITAL ELECTRONICS — FUNDAMENTAL NOTES

1. LOGIC FUNCTIONS & LOGIC GATES

- Logic gates are the basic building blocks of digital circuits.
- They operate on *binary values* — **0 (LOW) (FALSE)** and **1 (HIGH) (TRUE)**.

1.1 Basic Logic Gates

A) AND Gate

- Output is **1 only when all inputs are 1**.

Symbol



Truth Table

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

B) OR Gate

- Output is **1 if any input is 1**.

Symbol



Truth Table

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

C) NOT Gate

- Produces **inverse** of input.

Symbol



Truth Table

A	$Y = A'$
0	1
1	0

1.2 Universal Gates

A) NAND Gate

- NOT + AND
- Output is **0** only when all inputs are 1.

Symbol



Truth Table

A	B	$Y = (A \cdot B)'$
0	0	1
0	1	1
1	0	1
1	1	0

B) NOR Gate

- NOT + OR
- Output is **1** only when all inputs are 0

Symbol



Truth Table

A	B	$Y = (A + B)'$
0	0	1
0	1	0
1	0	0
1	1	0

1.3 XOR & XNOR Gates

A) XOR Gate

- Output is **1** if inputs are different.

Symbol



Truth Table

A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

B) XNOR Gate

- Output is **1** if inputs are same.

Symbol



Truth Table

A	B	$Y = (A \oplus B)'$
0	0	1
0	1	0

1	0	0
1	1	1

2. BOOLEAN ALGEBRA

Boolean algebra is used to analyze and simplify logic circuits.

2.1 Basic Boolean Operations

Operation	Symbol	Meaning
AND	$A \cdot B$	Both must be 1
OR	$A + B$	Any one must be 1
NOT	A'	Invert

2.2 Important Boolean Laws

A) Identity Laws

- $A + 0 = A$
- $A \cdot 1 = A$

B) Null Laws

- $A + 1 = 1$
- $A \cdot 0 = 0$

C) Idempotent Laws

- $A + A = A$
- $A \cdot A = A$

D) Inverse Laws

- $A + A' = 1$
- $A \cdot A' = 0$

E) Commutative Laws

- $A + B = B + A$
- $A \cdot B = B \cdot A$

F) Distributive Laws

- $A(B + C) = AB + AC$
- $A + BC = (A + B)(A + C)$

G) De Morgan's Theorems

1. $(A \cdot B)' = A' + B'$
2. $(A + B)' = A' \cdot B'$

2.3 Boolean Expression Simplification (Example)

Simplify:

$$Y = A \cdot B + A \cdot B'$$

$$Y = A(B + B')$$

$$\text{But } B + B' = 1$$

So:

$$Y = A \cdot 1 = A$$

3. DE MORGAN'S LAWS

De Morgan's laws help convert AND \leftrightarrow OR operations when a NOT (inversion) is applied to the entire expression.

These are essential for simplifying circuits and implementing designs using only **NAND** or **NOR** gates.

3.1 First De Morgan's Law

$$(A \cdot B)' = A' + B'$$

Meaning:

- The **complement of an AND** is equal to the **OR of the complements**.

Intuition:


If NOT is applied to an AND operation, you can distribute the NOT to each input, but AND becomes OR.

Truth Table Demonstration

A	B	A . B	(A . B)'	A'	B'	A' + B'
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

Both $(A \cdot B)'$ and $A' + B'$ produce the same output.

Logic Diagram

 

Both diagrams give identical results.

3.2 Second De Morgan's Law

$$(A + B)' = A' \cdot B'$$

Meaning:

- The **complement of an OR** is equal to the **AND of the complements**.

Intuition:

If NOT is applied to an OR operation, distribute the NOT, but OR becomes AND.

Truth Table Demonstration

A	B	A + B	(A + B)'	A'	B'	A' + B'
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

Both expressions match exactly.

3.3 Generalized De Morgan's Laws

These apply to expressions with more than two variables:

For AND:

$$(A \cdot B \cdot C \cdot D)' = A' + B' + C' + D'$$

For OR:

$$(A + B + C + D)' = A' \cdot B' \cdot C' \cdot D'$$

This is widely used in simplification.

3.4 Using De Morgan's Laws in Circuit Design

Converting a NAND implementation:

Since NAND = (AND)'

$$\text{NAND}(A, B) = (A \cdot B)' = A' + B'$$

So a NAND gate behaves like an OR gate with inverted inputs.

Converting a NOR implementation:

Since NOR = (OR)'

$$\text{NOR}(A, B) = (A + B)' = A' \cdot B'$$

So a NOR gate behaves like an AND gate with inverted inputs.

These transformations allow designers to build **entire circuits using only NAND or only NOR**, which is cost-effective in IC design.


4. COMBINATIONAL LOGIC CIRCUITS

Combinational circuits depend only on **current inputs**, not memory.

4.1 Half Adder

Performs **addition of two bits**.

Logic Diagram

 


Truth Table

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

4.2 Full Adder

Adds **three inputs**: A, B, Cin.

Logic Diagram

 

Truth Table

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{SUM} = A \oplus B \oplus \text{Cin}$$


$$\text{CARRY} = \text{Carry}_1 + (\text{SUM}_1 \cdot \text{Cin})$$

4.3 Multiplexer (MUX)

Selects **one input out of many**.

Example: 2-to-1 MUX

Logic Diagram

 

Symbol

 


Figure 1 - 2:1 Multiplexer

Truth Table

S	Y
0	I ₀
1	I ₁

Boolean Expression

$$Y = S' \cdot A_0 + S \cdot A_1$$

4.4 Decoder

Opposite of MUX — converts **n-bit input into 2ⁿ outputs**.

Example: 2-to-4 Decoder

A ₁	A ₀	Output
0	0	Y ₀ = 1
0	1	Y ₁ = 1
1	0	Y ₂ = 1
1	1	Y ₃ = 1

4.5 Encoder, Comparator, Parity Generator

(Brief definitions)

- **Encoder:** Converts many inputs → fewer outputs.
- **Comparator:** Compares two binary numbers.
- **Parity Generator:** Produces parity bit for error checking.